

Contents

Preface	vii
1. Introduction	1
1.1 What is an NMR Probe	1
1.1.1 The basic pulsed NMR experiment.	5
1.1.2 The head probe from a theoretical point of view.	9
1.1.2.1 The principle of reciprocity and the calculation of the induced emf	9
1.1.2.2 Losses	13
1.1.2.3 The sensitivity	16
1.2 What Probes for a Specific NMR Experiment	18
1.2.1 High resolution NMR in solution.	19
1.2.2 Solid state NMR.	20
1.2.3 Biomedical and biophysical applications.	21
2. Radio Frequency Components	23
2.1 The RF Parts of NMR Spectrometers and Scanners	23
2.2 Characterization of RF Components	26
2.2.1 Frequency range	26
2.2.2 Complex impedance and admittance	28
2.2.3 Impedance measurements and reflection coefficient	30
2.2.4 S-parameters	36
2.2.5 The Smith Chart	40
2.3 Electrical Properties of Materials	44
2.3.1 Resistance of metal conductors.	44
2.3.2 Losses in dielectric substrate.	48
2.4 Passive Linear Components at RF.	51
2.4.1 Conductors.	51
2.4.1.1 Round wire	52
2.4.1.2 Ribbon conductor.	53
2.4.1.3 Litz wire.	55
2.4.2 Cables and transmission lines.	58
2.4.2.1 Wave propagation and characteristic impedance.	59
2.4.2.2 Low-loss transmission lines	63
2.4.2.3 Attenuation in low-loss lines terminated by Z_c	65
2.4.2.4 Attenuation when the line is not terminated by its characteristic impedance Z_c	70
2.4.2.5 Impedance transformation	75

2.4.3	Discrete passive components.	81
2.4.3.1	Resistors.	81
2.4.3.2	Inductors (generalities).	82
2.4.3.3	The air-solenoid (high frequency model. Q optimization).	83
2.4.3.4	High frequency model of the air-solenoid.	90
2.4.3.5	Toroidal inductors.	91
2.4.3.6	Other inductors (single loop, printed spiral coil)	94
2.4.3.7	Choke inductor.	98
2.4.3.8	Adjustable inductor.	103
2.4.3.9	Capacitors (generalities)	104
2.4.3.10	Capacitors (high frequency model).	105
2.4.3.11	Fixed capacitor	107
2.4.3.12	Variable capacitor	108
2.4.3.13	Resonators	109
2.4.4	Distributed components made by transmission lines	116
2.5	Non-linear Devices (Diodes).	124
2.5.1	Silicon and Schottky P–N diodes.	125
2.5.2	PIN diodes.	127
2.5.2	Varactors.	127
2.6	Active Devices (Low Noise Amplifier or LNA).	128
2.6.1	Noise factor F and noise figure NF	128
2.6.2	LNA designs for NMR frequencies	131
2.7	Metamaterials (Flux Guides).	137
2.7.1	Magnetic metamaterials at RF	138
2.7.2	Components of a magnetic metamaterial	143
2.7.2.1	“Swiss-Rolls”	144
2.7.2.2	Ring planar resonators.	145
2.7.2.3	Transmission line network.	148
2.7.3	RF metamaterial designs	150
2.7.3.1	Flux compressors and flux guides.	151
2.7.3.2	Lenses	151
2.7.4	Dielectric resonators	152
3.	Introduction to Linear Network Analysis	155
3.1	Introduction to Network Theory.	156
3.1.1	Impedance and admittance matrices.	160
3.1.2	The transmission (ABCD) matrix.	162
3.1.3	The scattering matrix.	167
3.2	Linear Network Simulation of Probe Coil Circuits	168
3.2.1	NMRP: a simple tool for probe evaluation.	169
3.2.1.1	Simprobe: a linear probe network analyzer.	169

3.2.1.2	Building the Z matrix.	176
3.2.1.3	Analysis of simprobe outputs	179
3.2.1.4	Calculating inductances	185
3.2.1.5	Calculating current densities	186
3.2.1.6	Calculating resonant spectrum	188
3.2.1.7	Mutual inductance and current distribution	189
3.2.2	Other dedicated linear circuit analyzers.	194
4.	Interfacing the NMR Probe Head	197
4.1	Impedance Matching.	199
4.1.1	The Bode–Fano limit	199
4.1.2	Connected matching circuits	201
4.1.2.1	Basic L-matching circuits.	201
4.1.2.2	Series tuned/parallel matching	203
4.1.2.3	Parallel tuned/series matching	207
4.1.2.4	Efficiency of the capacitive matching circuits	212
4.1.2.5	Transmission line matching (remote matching).	214
4.1.2.6	Efficiency of transmission line matching networks	221
4.1.3	Flux coupled matching circuits	225
4.1.3.1	Theory of inductive matching.	228
4.1.3.2	Inductive matching with tuned coupling loop	230
4.1.3.3	Inductive matching with a non-tuned coupling loop	231
4.1.3.4	Inductive matching with fixed mutual and variable capacitor	233
4.1.3.5	Efficiency of the inductive coupling	235
4.1.3.6	Coupled resonators.	236
4.1.3.7	Flux concentrators.	238
4.2	Balancing the Probehead	243
4.2.1	Evidencing the electric losses effect	244
4.2.1.1	Experimental setup.	245
4.2.1.2	Expected sensitivity	246
4.2.1.3	Frequency shifts	248
4.2.1.4	Q factors	250
4.2.2	Evidencing the electric losses: the antenna effect	251
4.2.3	Symmetrical capacitive coupling networks.	254
4.2.3.1	Splitting the matching capacitor.	254
4.2.3.2	A versatile capacitive balanced matching network.	256
4.2.3.3	Capacitive bridge.	264
4.3	Summary of useful matching circuits	265
4.4	Accessories	268
4.4.1	Transmit/receive (TR) switches.	268
4.4.2	Damping circuits.	270

4.4.3	Baluns and cable traps	275
4.4.3.1	LC-balun.	277
4.4.3.2	The 4 : 1 $\lambda/2$ balun transformer.	278
4.4.3.3	Broadband balun transformers.	279
4.4.3.4	Tuned cable traps.	281
4.5	Interfacing the Probe to a Low Noise Amplifier (LNA).	284
4.6	Ultra-broadband and Ultrafast Recovery Probes.	289
4.6.1	Delay line ultra-broadband NMR probe	290
4.6.2	Transmission line ultra-broadband NMR probe	292
4.6.3	Non-resonant probe circuit.	293
5.	Quadrature Driving	295
5.1	Interfacing the Quadrature Probehead to the Console.	297
5.2	Quadrature Hybrids	302
5.2.1	$\lambda/4$ transmission line hybrid.	302
5.2.2	$\lambda/8$ transmission line hybrid.	309
5.2.3	Lumped element quadrature hybrids.	315
5.2.3.1	Quarter-wave hybrid equivalent.	316
5.2.3.2	$\lambda/8$ hybrid equivalent.	319
5.2.4	Frequency response of the quad hybrids.	320
5.3	180° Hybrid.	325
5.3.1	The 180° rat-race hybrid.	326
5.3.2	Using the rat-race hybrid 180° in quadrature NMR.	334
5.3.3	Lumped element equivalent of the 180° hybrid.	336
5.3.4	Frequency response of the 180° ring hybrids.	338
5.4	Other 90° Hybrids.	341
6.	Multiple Frequency Tuning	345
6.1	Shunting Methods.	350
6.1.1	Dual frequency switching circuits.	350
6.1.2	Practical double tuned circuits.	355
6.1.3	Multiple tuning of a single coil.	361
6.1.4	Balancing the shunting configurations.	367
6.1.4.1	Approximate balanced circuit.	368
6.1.4.1	Multiple-frequency full balancing circuit.	370
6.2	Multiple-pole Circuits.	374
6.2.1	Approximate double-pole network component values	378
6.2.2	Exact solutions	382
6.2.3	Multiple-pole tuning for more than two frequencies	383
6.2.4	Balancing the multiple-pole circuits	384
6.2.4.1	Inductive coupling.	384
6.2.4.2	The null-point method.	386

6.3 Coupling Tank Circuits.	388
6.3.1 Coupled identical resonators.	392
6.3.2 Coupled resonators having the same resonance frequency but different L/C ratio.	395
6.3.3 General case (different coupled resonators).	396
6.3.4 Fluxed coupled resonators.	398
6.3.5 Special case of a short circuited coil.	402
6.3.6 Π -network configuration.	403
6.3.7 Summary of coupled resonator properties.	407
6.4 Efficiency of Multiple Tuned NMR Probe.	411
6.4.1 Efficiency of shunting methods.	411
6.4.2 Efficiency of multiple pole circuits.	415
6.4.3 Efficiency of coupled resonant circuits.	421
6.5 Interfacing the Multiple Frequency Resonator to the Spectrometer . .	422
6.6 Is the Q Factor Representative of the Sensitivity?	424
7. Magnetic Field Amplitude Estimation	427
7.1 The Biot–Savart Approximation.	427
7.1.1 Magnetic field produced by straight wires.	429
7.1.2 Magnetic field produced by a loop.	432
7.2 Effective Field for NMR Experiments.	436
7.3 Estimation of the Current Distribution.	441
7.3.1 Limits and usefulness of the thin wire approximation.	441
7.3.2 Current distribution in the isolated flat strip.	443
7.3.3 Proximity effects.	452
7.3.3.1 Two coplanar strips.	452
7.3.3.2 Three or more strips.	455
7.3.3.3 Wire in proximity of a conductive plane.	456
7.3.4 Current density in round wires.	459
7.3.5 Concluding remarks.	461
7.4 Survey of Modern Electromagnetic Simulation Methods.	462
8. Homogeneous Resonators	467
8.1 Axial Resonators.	469
8.1.1 Magnetic field amplitude.	469
8.1.2 Approximations of the spherical uniform current density.	473
8.1.2.1 Helmholtz coil.	473
8.1.2.2 Four coil configuration.	475
8.1.2.3 Guidelines for a practical design of Helmholtz probes and four coil probes.	478
8.1.3 Solenoid types.	480
8.1.3.1 The solenoid coil.	480

8.1.3.2	The loop gap.	485
8.1.4	Practical designs of solenoid type coils	490
8.1.4.1	A microcoil for static magnetic field mapping	490
8.1.4.2	A 0.4 ml high sensitivity phosphorous coil (162 MHz)	491
8.1.4.3	A 150 ml double tuned (1H/31P)coil operating at 4.7 T	493
8.2	Transverse Resonators.	498
8.2.1	Magnetic field amplitude.	498
8.2.2	The saddle-shaped coil.	501
8.2.2.1	The optimum geometry and RF magnetic field	501
8.2.2.2	A practical design.	505
8.2.3	UHF saddle coil-like resonators.	509
8.2.3.1	The Alderman–Grant coil, a version of the slotted cylinder.	511
8.2.3.2	Coupling the Alderman–Grant resonator to the spectrometer, a practical design.	515
8.2.3.3	Shielding the UHF saddle coil-like resonators.	520
8.2.4	The birdcage resonator.	527
8.2.4.1	RF field map of the $k = 1$ mode.	528
8.2.4.2	Network analysis of the birdcage circuit	534
8.2.4.3	Estimation of the current in a birdcage coil	541
8.2.4.4	Estimation of the tuning capacitance.	548
8.2.5	Practice of the birdcage.	552
8.2.5.1	Tuning the birdcage resonator.	552
8.2.5.2	Asymmetry effects.	556
8.2.5.3	Interfacing the birdcage to the spectrometer	560
8.2.5.4	A practical design.	562
8.2.6	Practical design of a quadrature birdcage.	570
8.2.6.1	Designing and adjusting the quadrature resonator for quadrature operation	572
8.2.6.2	Interfacing the resonator to the console	575
8.2.6.3	Design of the shield.	577
8.2.6.4	Evaluation of the probe	578
8.2.7	Double tuning the birdcage resonator.	579
8.2.7.1	Pole insertion methods.	580
8.2.7.2	Alternate rung method.	581
8.2.7.3	Four ring double resonant birdcage	583
8.2.7.4	Crossed-coil resonators	585
8.2.7.5	A practical design.	587
8.3	Transmission lines resonator	592
8.3.1	TEM resonators.	592

8.3.2 Split transmission line resonators.	597
9. Heterogeneous Resonators	601
9.1 The Basic Surface Coil.	601
9.1.1 The simple loop magnetic field distribution.	603
9.1.1.1 “Ideal” case.	603
9.1.1.2 Effect of inductive coupling.	606
9.1.2 Practical design guidelines.	611
9.1.2.1 How many turns?	611
9.1.2.2 Spiral windings.	611
9.1.2.3 Non-circular winding shapes	616
9.1.2.4 Wiring shape	618
9.1.2.5 Opened resonators	622
9.1.3 Surface coils for ultra high frequency	623
9.1.3.1 Segmented loop.	623
9.1.3.2 The crossover coil.	625
9.1.3.3 Split ring resonator (common mode).	626
9.1.3.4 Microstrip coils (differential mode)	628
9.1.4 Superconducting surface coils.	630
9.1.5 Interfacing the coil to the spectrometer	632
9.2 Extending the Observed Volume (Multi-Ring Coils).	634
9.2.1 Coaxial rings.	634
9.2.1.1 RF field profiling.	634
9.2.1.2 X-observed, proton decoupled system	637
9.2.2 Array coils.	640
9.3 The Surface Coil as Receive-Only Probe	643
9.3.1 Passive decoupling	644
9.3.2 Active decoupling	651
10. Probe Evaluation and Debugging	655
10.1 Instrumentation.	656
10.1.1 The pick-up coil	656
10.1.2 Impedance bridge	657
10.1.3 Power divider, hybrid, and directional coupler	660
10.1.4 Sweep generator, crystal detector, and spectrum analyzer.	662
10.1.5 Scalar and vector network analyzer	665
10.1.5.1 Transmission/reflection and <i>S</i> -parameters test sets	666
10.1.5.2 Calibration	667
10.1.6 Other impedance measuring instruments	670
10.2 Characterization of a Transmission Line.	670
10.2.1 Velocity coefficient.	671
10.2.2 Evaluation of the characteristic impedance	672

xviii	<i>NMR Probeheads for Biophysical and Biomedical Experiments</i>	
	10.2.3 Estimation of the loss parameters	674
	10.3 Noise Figure Measurement.	674
	10.4 Evaluating the Probe on the RF Workbench.	678
	10.4.1 Matching the probe input impedance to 50 Ω	678
	10.4.2 Evaluation of the Q factor.	680
	10.4.3 B_1/\sqrt{P} evaluation methods.	684
	10.5 Evaluating the Probe on the NMR Instrument	686
	Appendix A. Physical Constants and Useful Formulae.	691
	Bibliography.	709
	<i>Index</i>	739